

ELT3207 Meas. & Digital Control Basics


Lecture 4: Data Acquisition Systems

Hoang Gia Hung


Faculty of Electronics and Telecommunications

University of Engineering and Technology, VNU Hanoi


Introduction

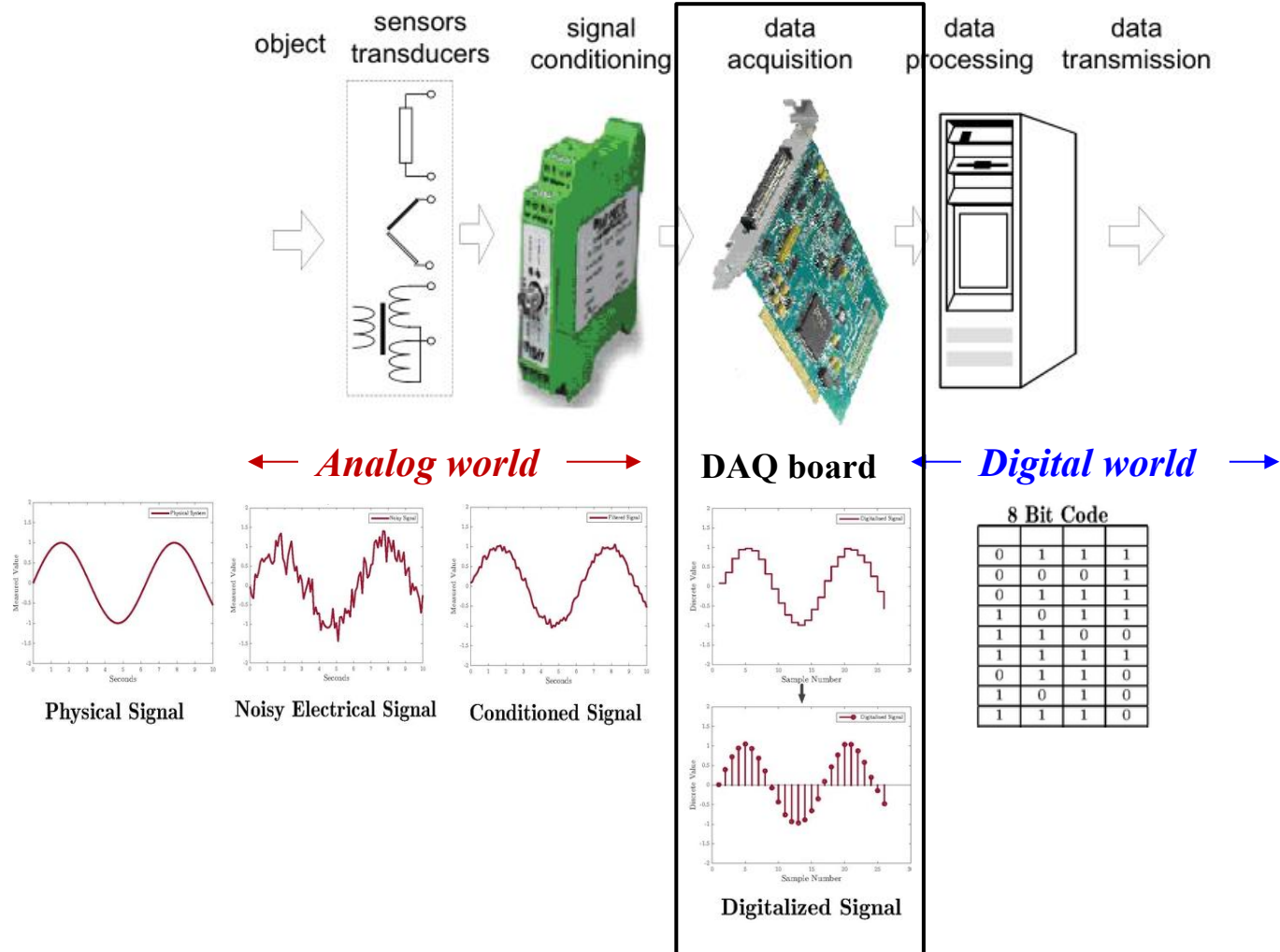

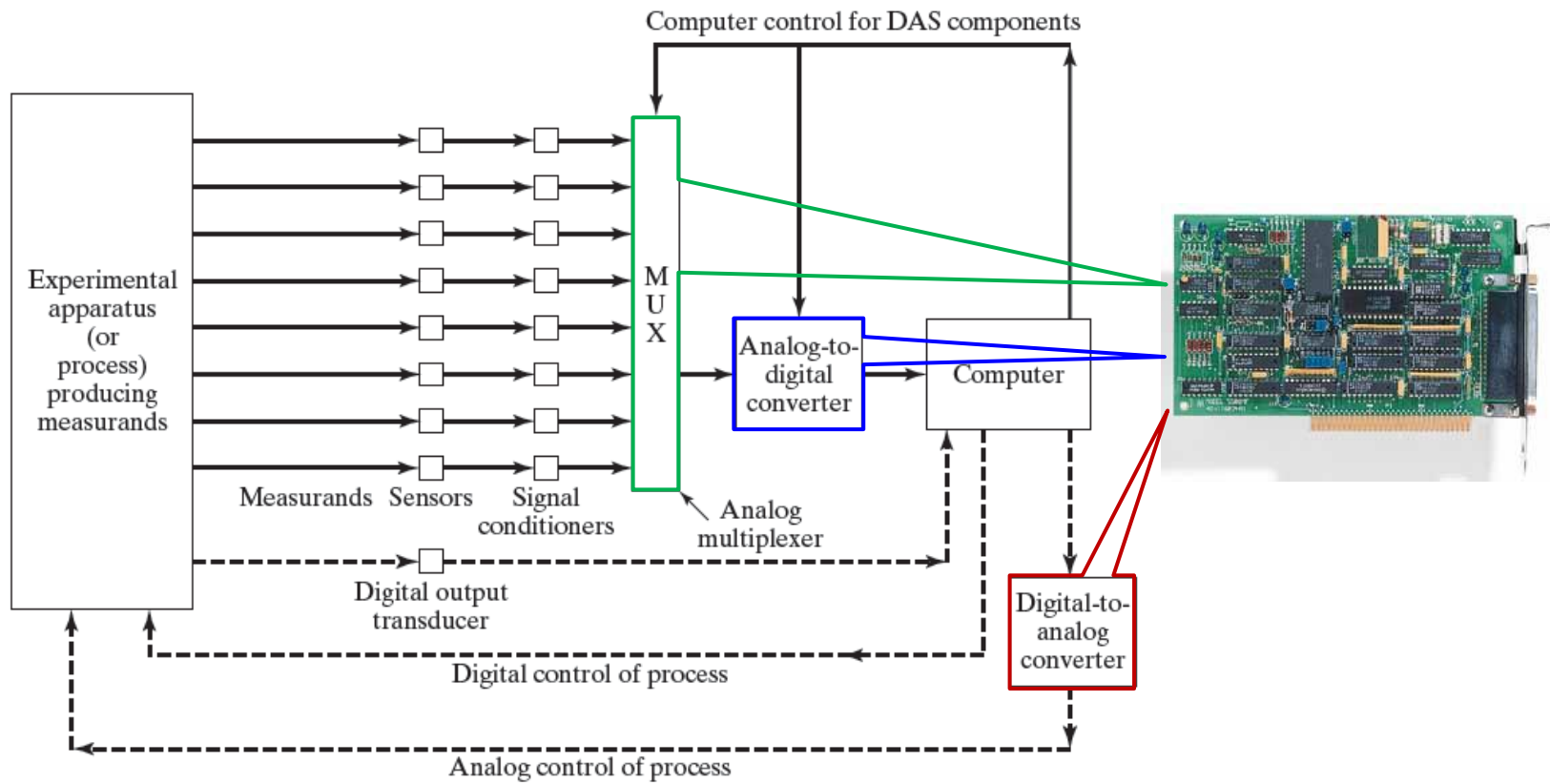Schematic of a computerized measurement & control system




Multiplexer

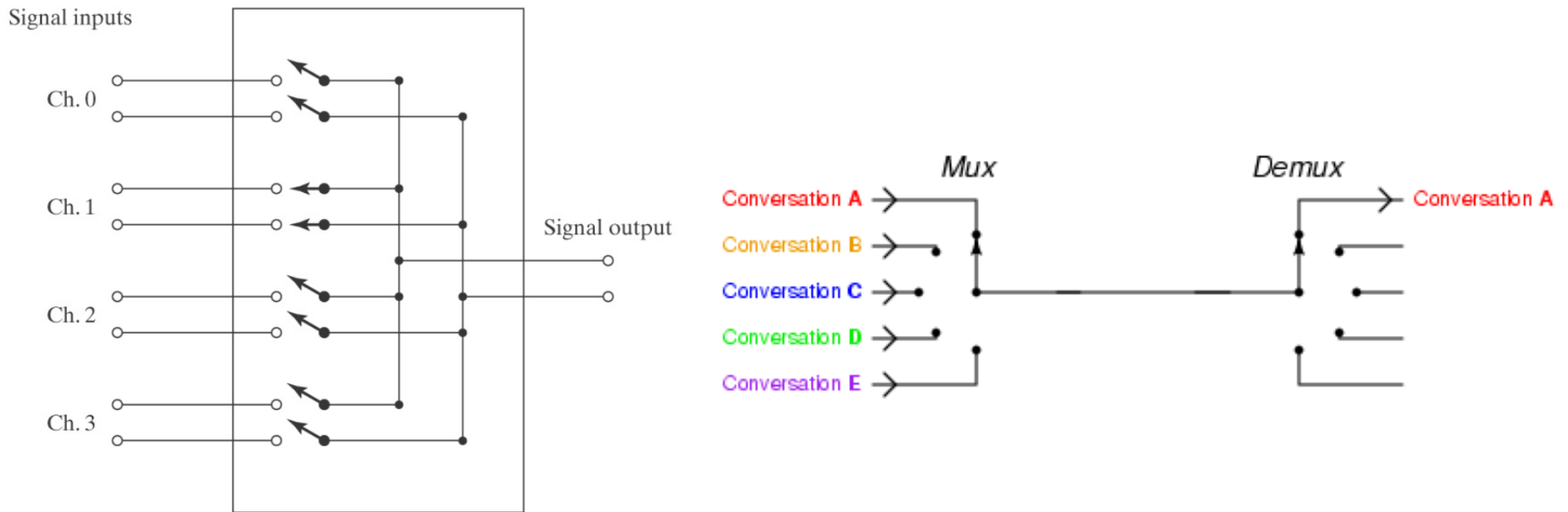

- ❑ Multiplexer (**MUX**): a device that selects one of many analog or digital data sources and outputs that source into a single channel.
- ❑ Demultiplexer (**DEMUX**) a device that that selects one of many data-output-lines and connects the selected output line to one single input.
 - A multiplexer is often used with a complementary demultiplexer on the receiving end.

Basics of Analog-to-Digital Conversion

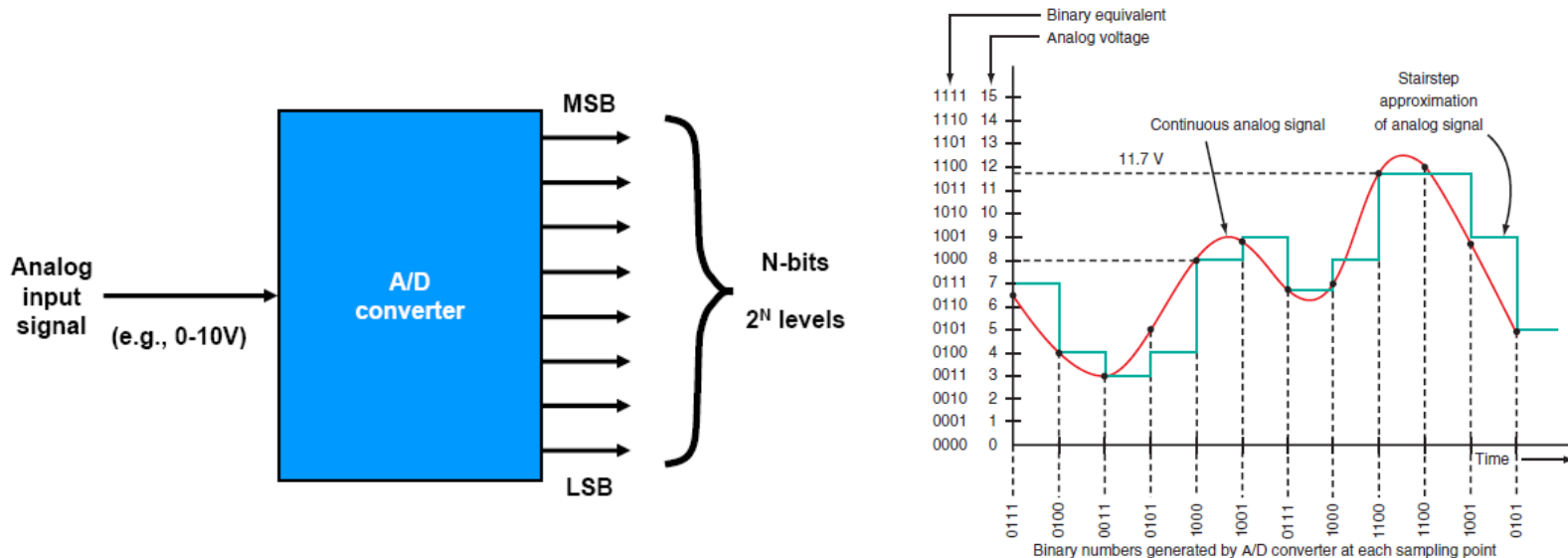

- ❑ A/D: the process of turning an analog voltage into a digital number. The device performing this function is called an ADC.
 - The digital number represents the input voltage in discrete steps with finite **resolution**.
 - ADC resolution is determined by the number of bits that represent the digital number.
 - **Example:** an 8-bit converter with a full-scale voltage of 10V will give you a resolution of $10V/256$ which is 39.1 mV.

ADC process


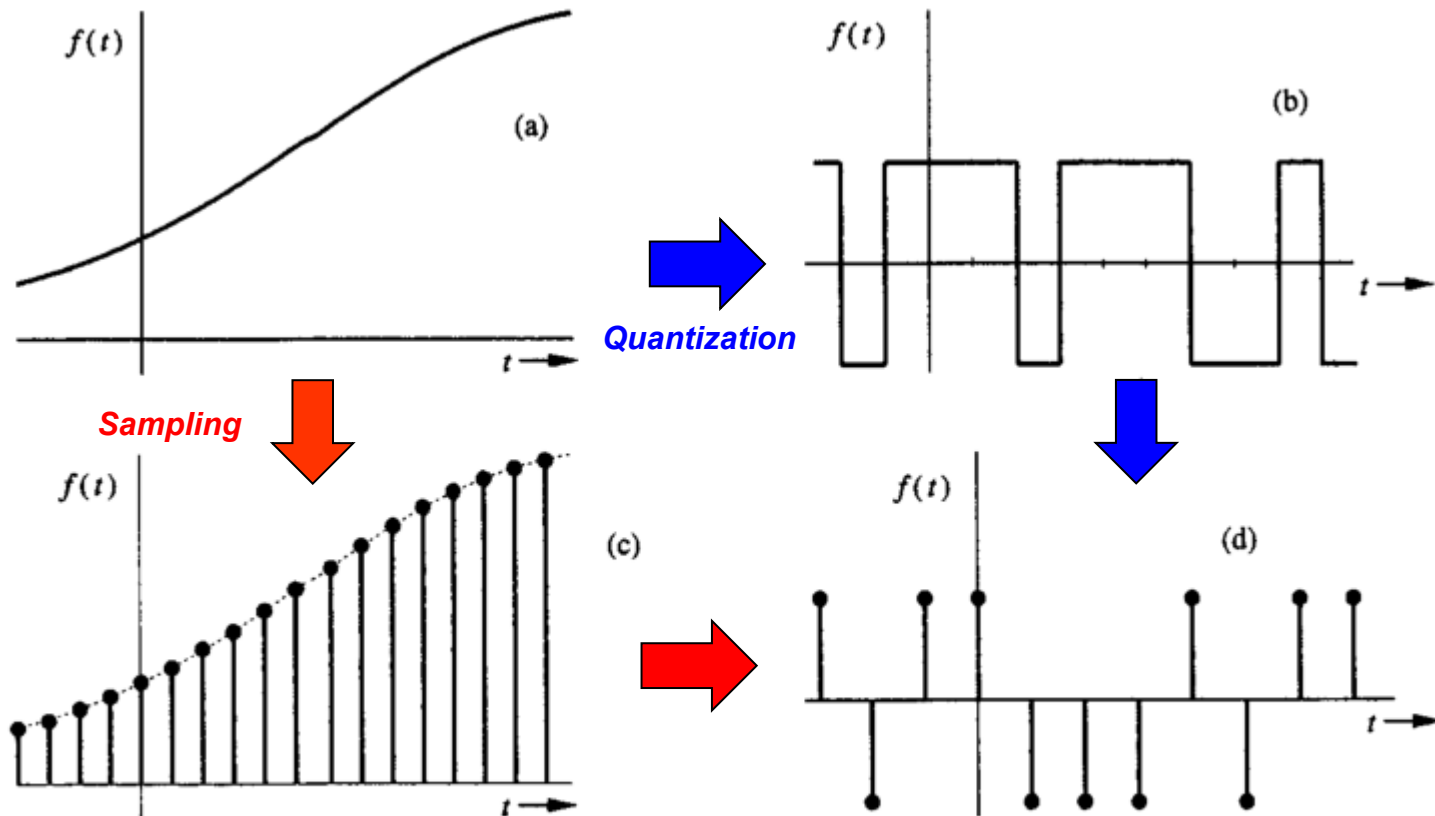
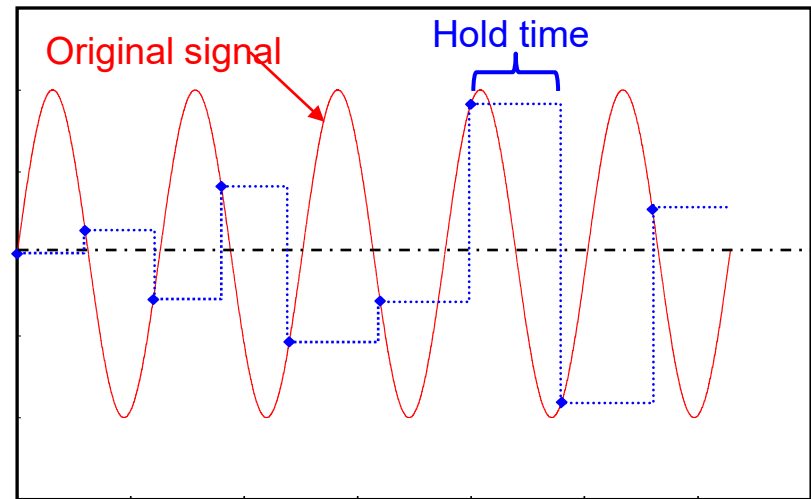


Fig. 1.5 Examples of Signals: (a) analog, continuous-time (b) digital, continuous-time (c) analog, discrete-time (d) digital, discrete-time.



- The terms continuous-time and discrete-time qualify the nature of signal along the time (horizontal) axis while the terms analog and digital qualify the nature of signal amplitude (vertical axis).

Sampling

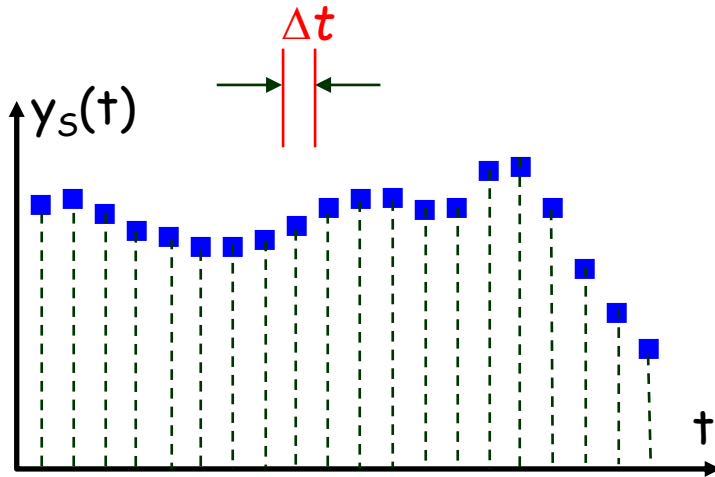





- ❑ Sampling interval $\Delta t \rightarrow$ sampling rate: $f_s = \frac{1}{\Delta t}$.
- ❑ Almost any analog to digital converter employ sample-and-hold technique, which holds each sample value (voltage) until the next pulse occurs.
 - The sampling and hold unit is necessary because the A/D converter requires a finite amount of time.

Aliasing and sampling theorem

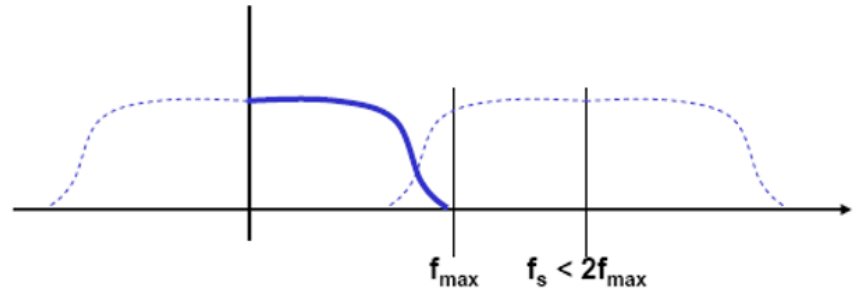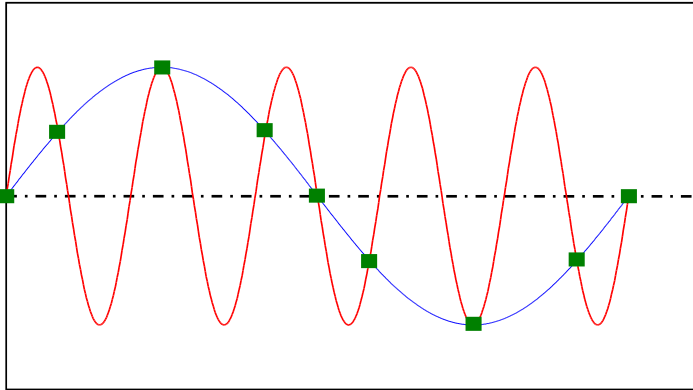

- **Aliasing**: an effect that causes different signals to become indistinguishable (or aliases of one another) when sampled.
- **Sampling theorem**: the sampling rate must be greater than twice the highest-frequency component of the original signal in order to reconstruct the original signal correctly, i.e. $f_s > 2f_m$, where f_m is the signal frequency (or the maximum signal frequency if there is more than one frequency in the signal).

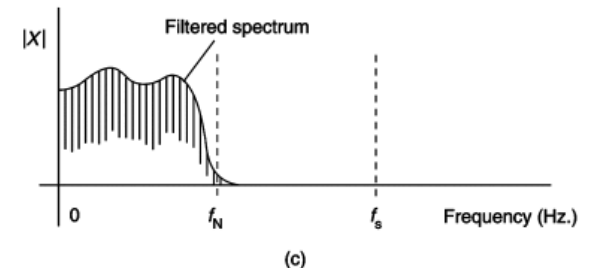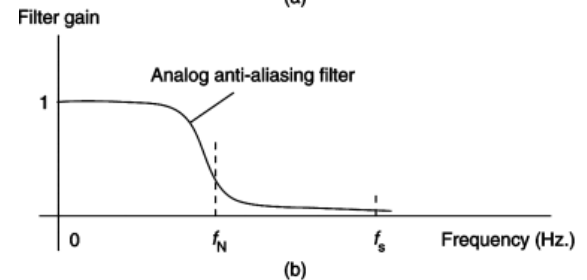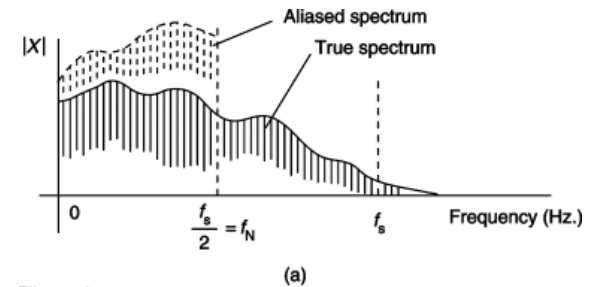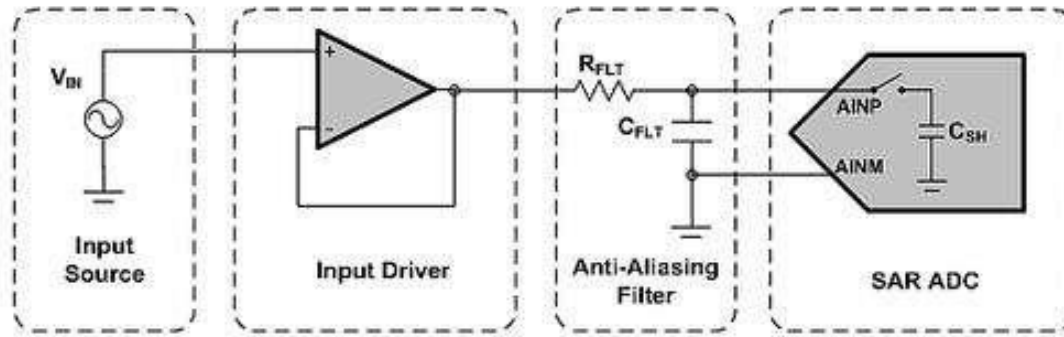Practical application of sampling theorem



- How does one avoid this alias phenomenon when sampling a signal of **unknown** frequency content?
 - ✓ Assign a sample rate so large that the measured signal does not have significant amplitude content above the Nyquist freq.
 - ✓ Pass the signal through a low-pass filter (**AAF**) based on the **maximum frequency of interest** prior to sampling.
- **Waveform Fidelity**: the sampling theorem ensures that there will be no aliasing associated with frequency content, it does not address the waveform distortion.
 - ✓ E.g., Super Audio CD (SACD) format recordings. As a **general rule** waveform fidelity is acceptable for $f_s \geq 5f_m$ to $10f_m$ depending on the application.

Quantization basics

- Quantization is the process to convert the input voltage range into $Q = 2^N$ bands to encode a continuous analog signal to discrete digital levels.

- Quantization Interval:


$$\Delta V = \frac{V_{ru} - V_{rl}}{Q}$$

- Quantization Error:

$$e_q^{\max} = \pm \frac{\Delta V}{2(V_{ru} - V_{rl})} \times 100\%$$

and is treated as an uncertainty, commonly referred to as **input resolution error**.

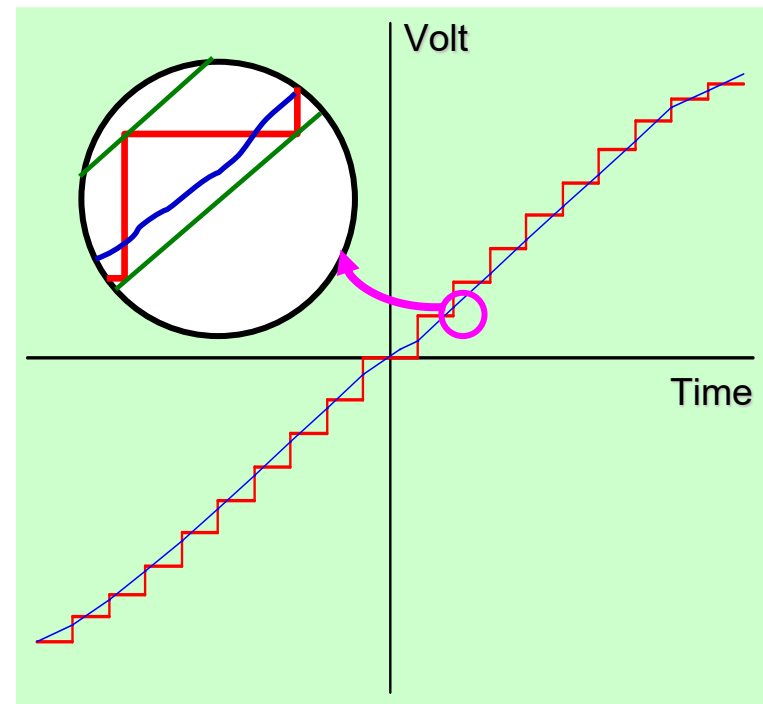- Saturation error** occurs if $V_i > V_{ru}$ or $V_i < V_{rl}$ and is considered a mistake which should have been avoided.



Quantization output encoding

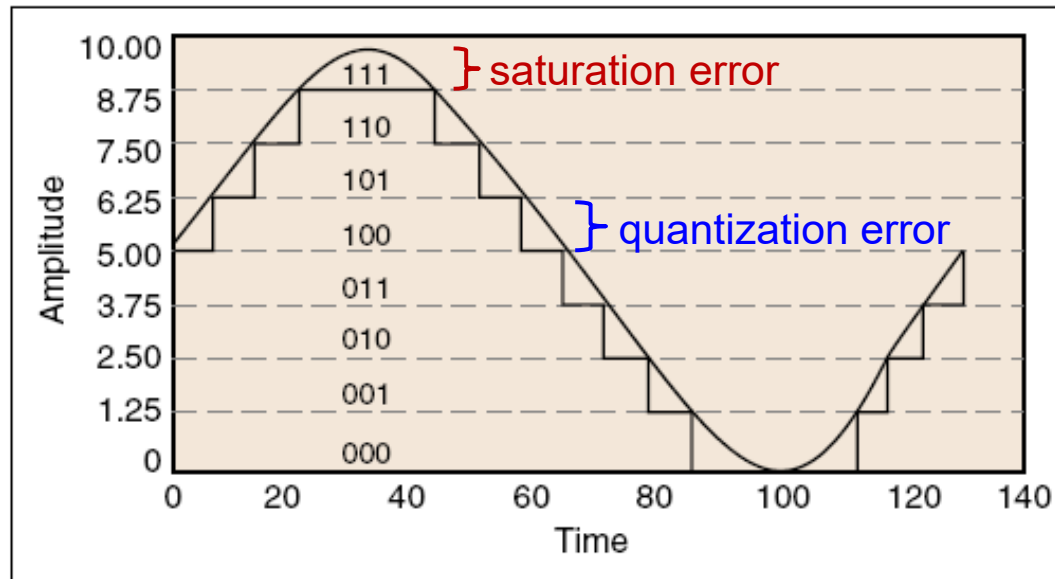


Figure 3. Digitized Sine Wave with a Resolution of Three Bits



□ There are a number of ways to encode the digital output of ADCs

➤ **Binary encoding:** N bits represent 2^N possible values for the output $\rightarrow N$ determines the resolution/quantization interval of the output: $LSB = \frac{V_{ru} - V_{rl}}{2^N}$.

Bits	1	2	6	8	10	12
$2^N =$	2	4	64	256	1024	4096
Res. %	50	25	1.6	0.39	0.1	0.024

Quantization & binary encoding (cont.)

- ❑ **Input range:** can be unipolar or bipolar
 - A **unipolar** converter can only respond to analog inputs with the same sign
 - **Bipolar** converters can convert both positive and negative analog inputs
- ❑ In general, the output of an ADC has 2^N possible values, where N is the number of bits used to represent the digital output.
 - The 1-bit device has two possible output states (0,1); the 2-bit device has 4 possible output states (00, 01, 10, and 11 in binary representation).
 - A comparator is the most basic 1-bit ADC

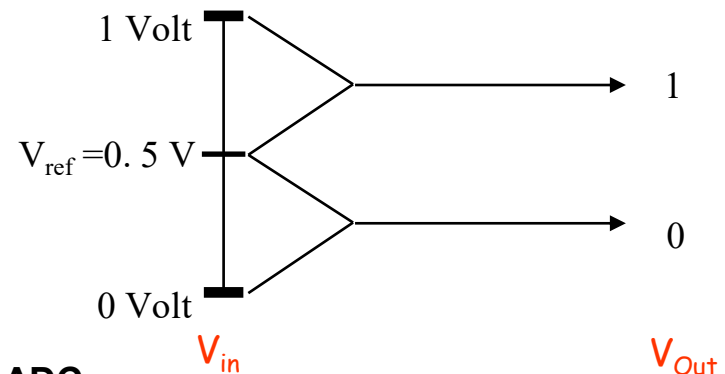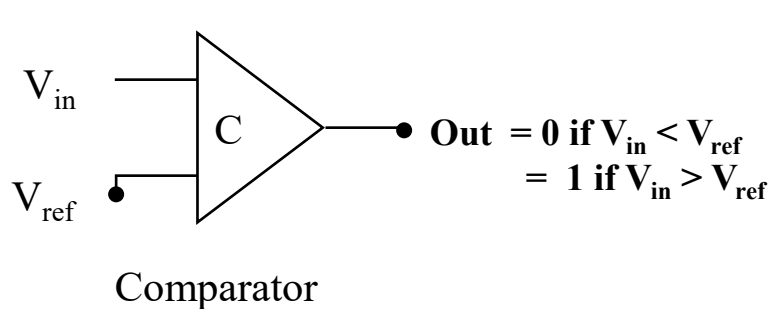

• This is a 1-bit Flash ADC

$$\text{Increment (resolution)} = \frac{1}{2^1} = 0.5 \text{ V}$$

Quantization & encoding: example

- ❑ A 4-bit single-slope integrating ADC has an input range of 0 to 10 V. Compute the digital output for an analog input of 6.115V?

- ❑ **Solution:**

- The incremental voltage increase in each clock tick is $(10 - 0)/2^4 = 0.625(V) \rightarrow$ the integrator voltage at the end of each clock tick: $0.625 \times 1 = 0.625$, $0.625 \times 2 = 1.250$, ..., $0.625 \times 10 = 6.250 > 6.115 \rightarrow$ stop counter $\rightarrow$ the output of the converter is 10, which has the value 1010 when expressed in binary.

- Generalization: $D = \text{int} \left\{ \frac{V_i - V_{rl}}{V_{ru} - V_{rl}} 2^N \right\} = \text{int} \left\{ \frac{6.115 - 0}{10} 2^4 \right\} = \text{int}(9.78) = 10.$



- ❑ A 12-bit A/D converter has an input range of -10 to + 10 V. Find the input resolution error of the converter for the analog input. What should we do if the input voltage is 0.1(V)?

- ❑ **Solution:**

- The input resolution error is $\pm 0.5 \left[\frac{10 - (-10)}{2^{12}} \right] = \pm 0.00244 \text{ V}.$

- If the input voltage is 0.1 V (which has a magnitude at the low end of the input range), the quantization error would then represent $\pm 2.5\%$ of the reading, which is probably not acceptable. The solution to this problem is to amplify the input (with some well-defined gain such as 10) before the signal enters the converter.

Single-slope integrating converter

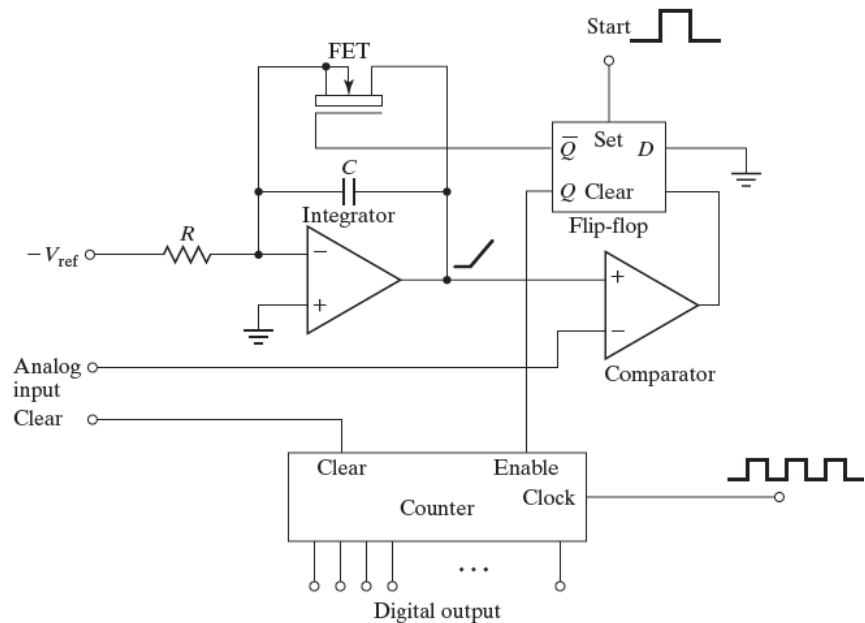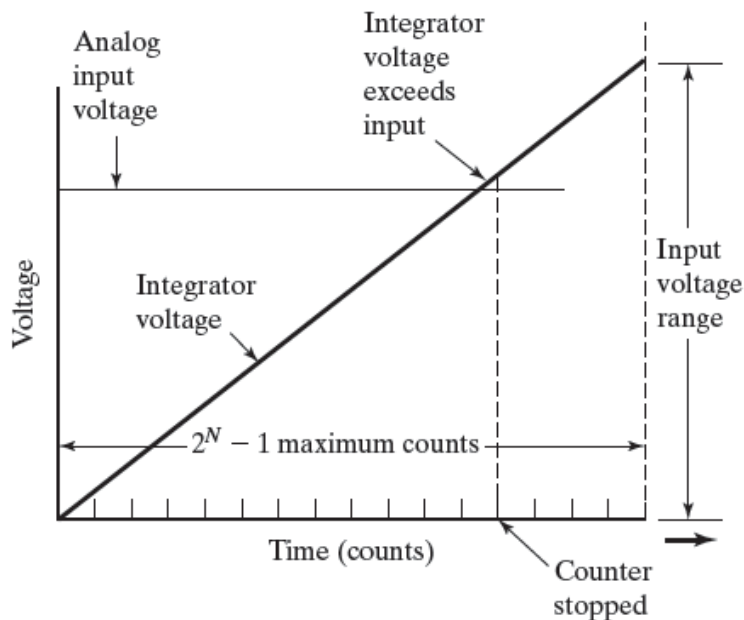

- A fixed reference voltage is used to charge an integrator at a **constant rate** → the integrator output voltage will then increase **linearly** with time, and is compared continuously with the analog input voltage using a comparator.
- A digital counter is started at the same time that the charging is begun.
- When the integrator voltage exceeds the analog input voltage, the digital clock is stopped → the count is the digital output of the A/D converter.

Example

- ❑ A 4-bit single-slope integrating ADC has an input range of 0 to 10 V. Compute the digital output for an analog input of 6.115V?

- ❑ **Solution:**

- The incremental voltage increase in each clock tick is $(10 - 0)/2^4 = 0.625(V) \rightarrow$ the integrator voltage at the end of each clock tick: $0.625 \times 1 = 0.625$, $0.625 \times 2 = 1.250$, ..., $0.625 \times 10 = 6.250 > 6.115 \rightarrow$ stop counter $\rightarrow$ the output of the converter is 10, which has the value 1010 when expressed in binary.

- **Generalization:** $D = \text{int} \left\{ \frac{V_i - V_{rl}}{V_{ru} - V_{rl}} 2^N \right\} = \text{int} \left\{ \frac{6.115 - 0}{10} 2^4 \right\} = \text{int}(9.78) = 10.$


- ❑ A 12-bit A/D converter has an input range of -10 to + 10 V. Find the input resolution error of the converter for the analog input. What should we do if the input voltage is 0.1(V)?

- ❑ **Solution:**


- The input resolution error is $\pm 0.5 \left[\frac{10 - (-10)}{2^{12}} \right] = \pm 0.00244 \text{ V}.$

- If the input voltage is 0.1 V (which has a magnitude at the low end of the input range), the quantization error would then represent $\pm 2.5\%$ of the reading, which is probably not acceptable. The solution to this problem is to amplify the input (with some well-defined gain such as 10) before the signal enters the converter.

Other common types of ADC

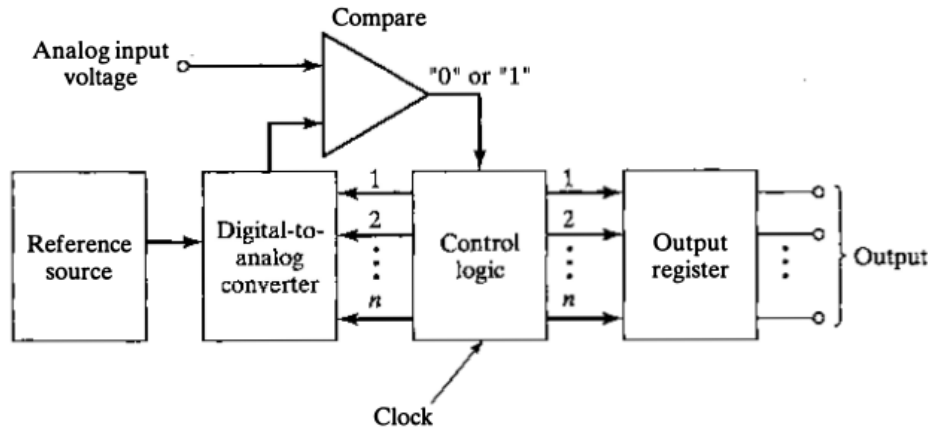


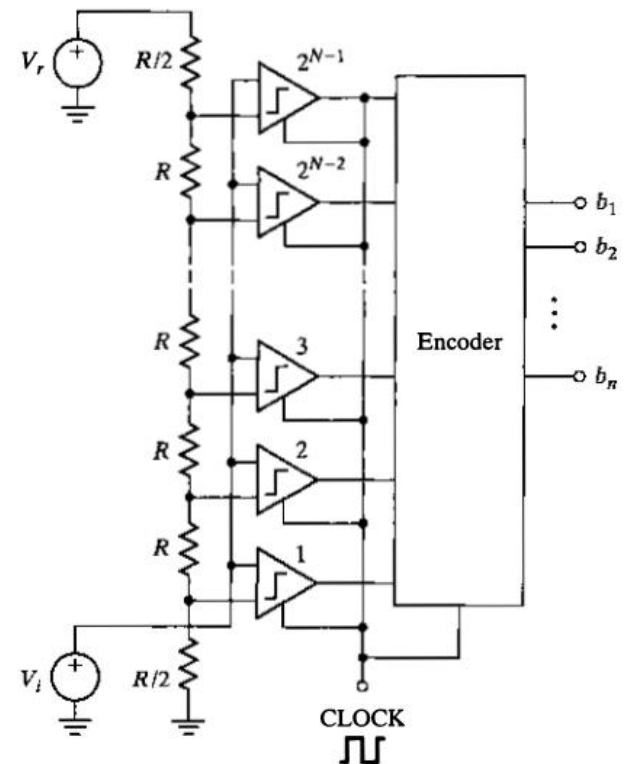- The most common type is the **successive-approximations converter**, in which a series of known analog voltages are created and compared to the analog input voltage.
- In the first trial, a voltage interval of one-half the input span is compared with the input voltage → determines the MSB.




- The fastest type of A/D converter is the **parallel** or **flash** A/D converter where the conversion process is completed in a single step.
- Parallel converters require a large number of components (e.g., $2^N - 1$ comparators).

Digital-to-Analog Conversion (DAC)

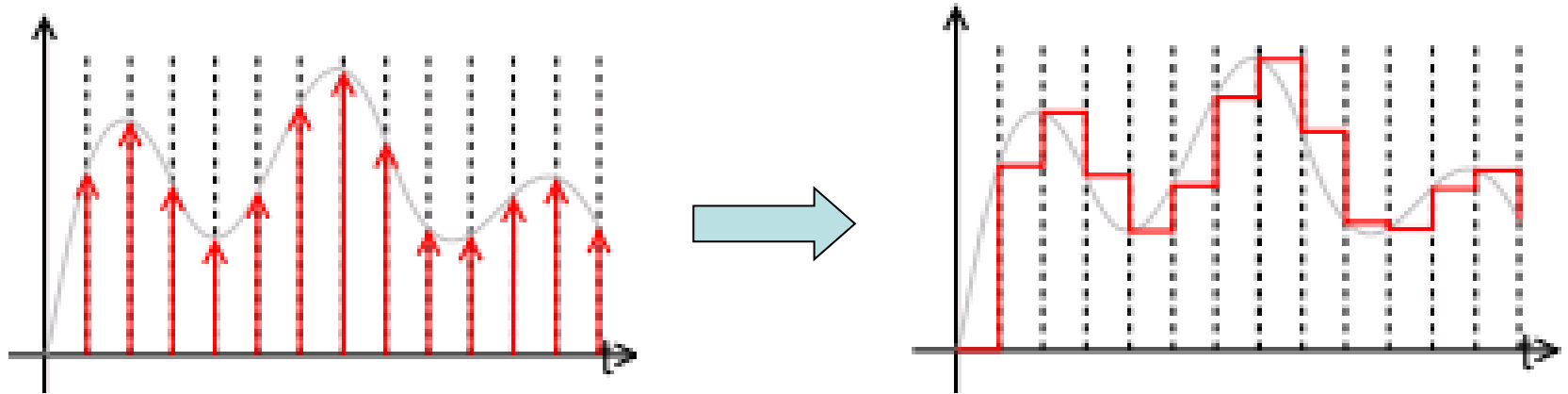

- ❑ The DAC fundamentally converts finite-precision numbers into a physical quantity, usually an electrical voltage.
 - Normally the output voltage is a linear function of the input number.
 - These numbers are usually updated at uniform sampling intervals and can be thought of as numbers obtained from a sampling process.
- ❑ Output is a sequence of piecewise constant values or rectangular pulses → there is an inherent effect of the zero-order hold on the effective frequency response of the DAC resulting in a mild roll-off of gain at the higher frequencies.

A Simple Digital-to-Analog Converter

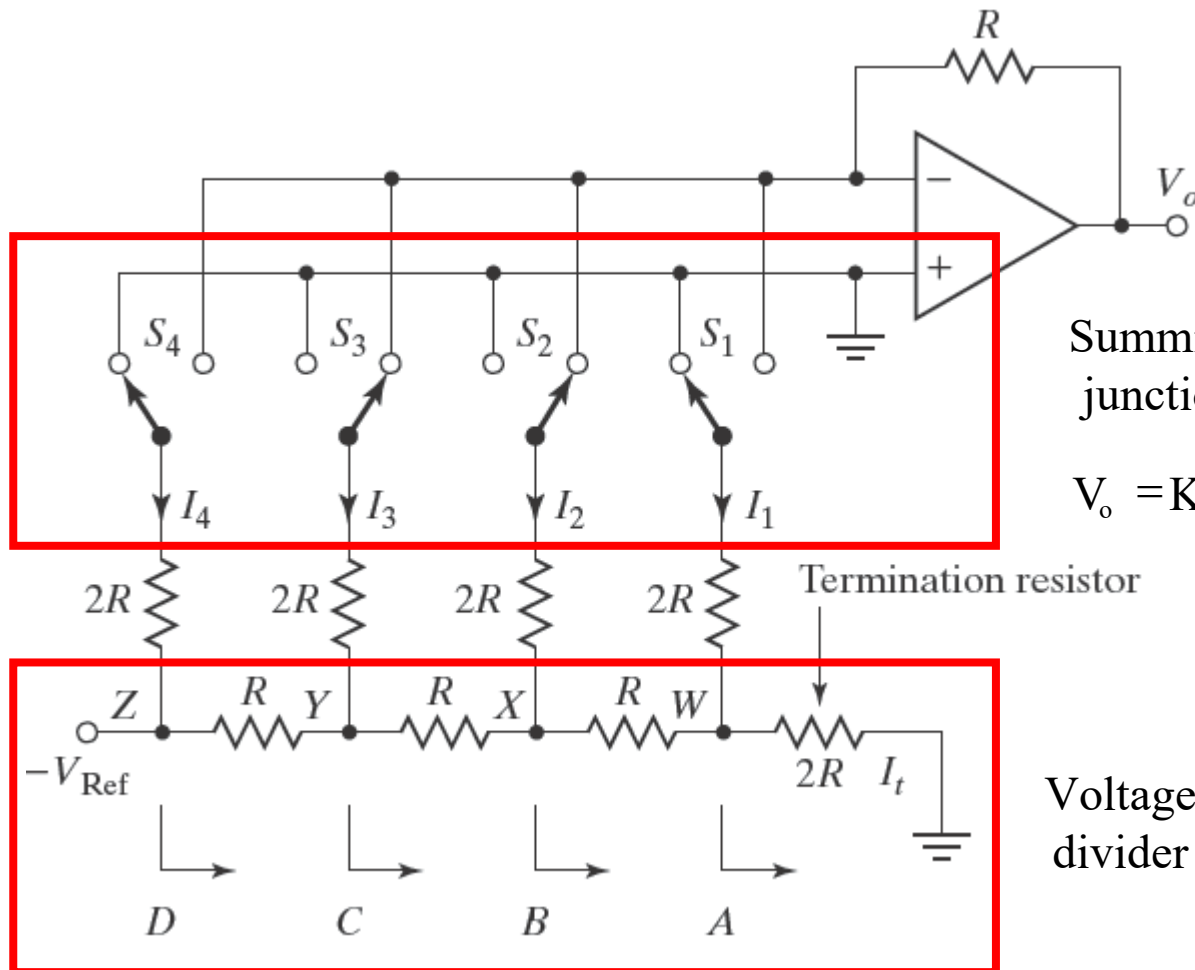





Summing
junction

$$V_o = K(S_4 \cdot 2^3 + S_3 \cdot 2^2 + S_2 \cdot 2^1 + S_1 \cdot 2^0)$$


Voltage
divider

- 4-bit DAC: the resulting analog output voltage will be proportional to the digital input number.


Putting all together

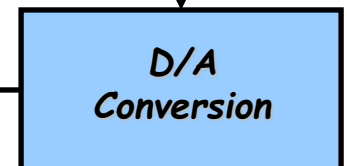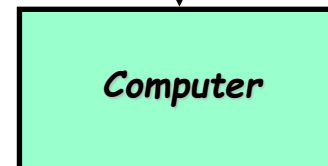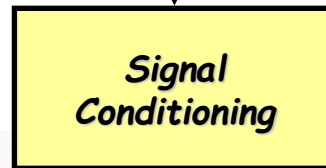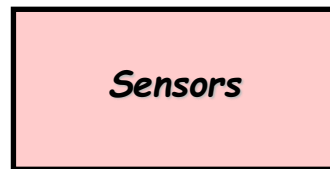

Feedback

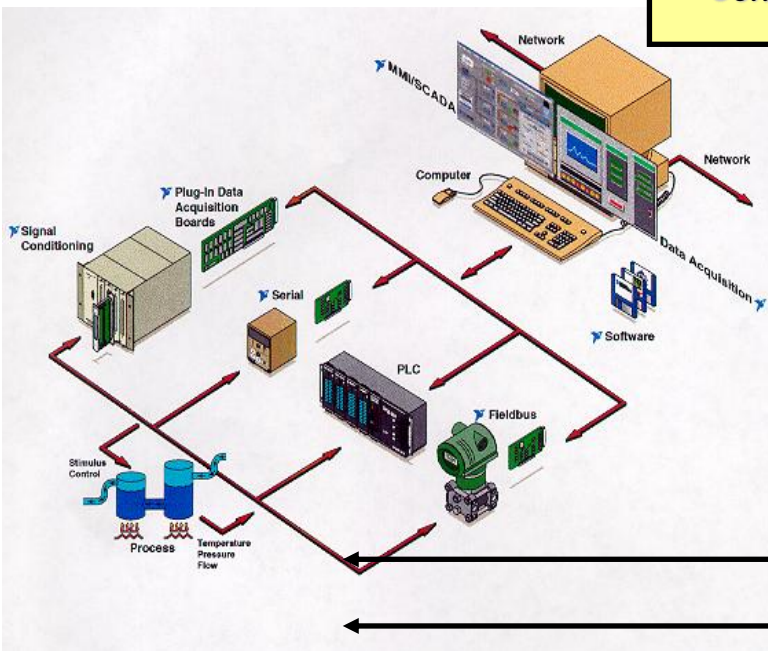

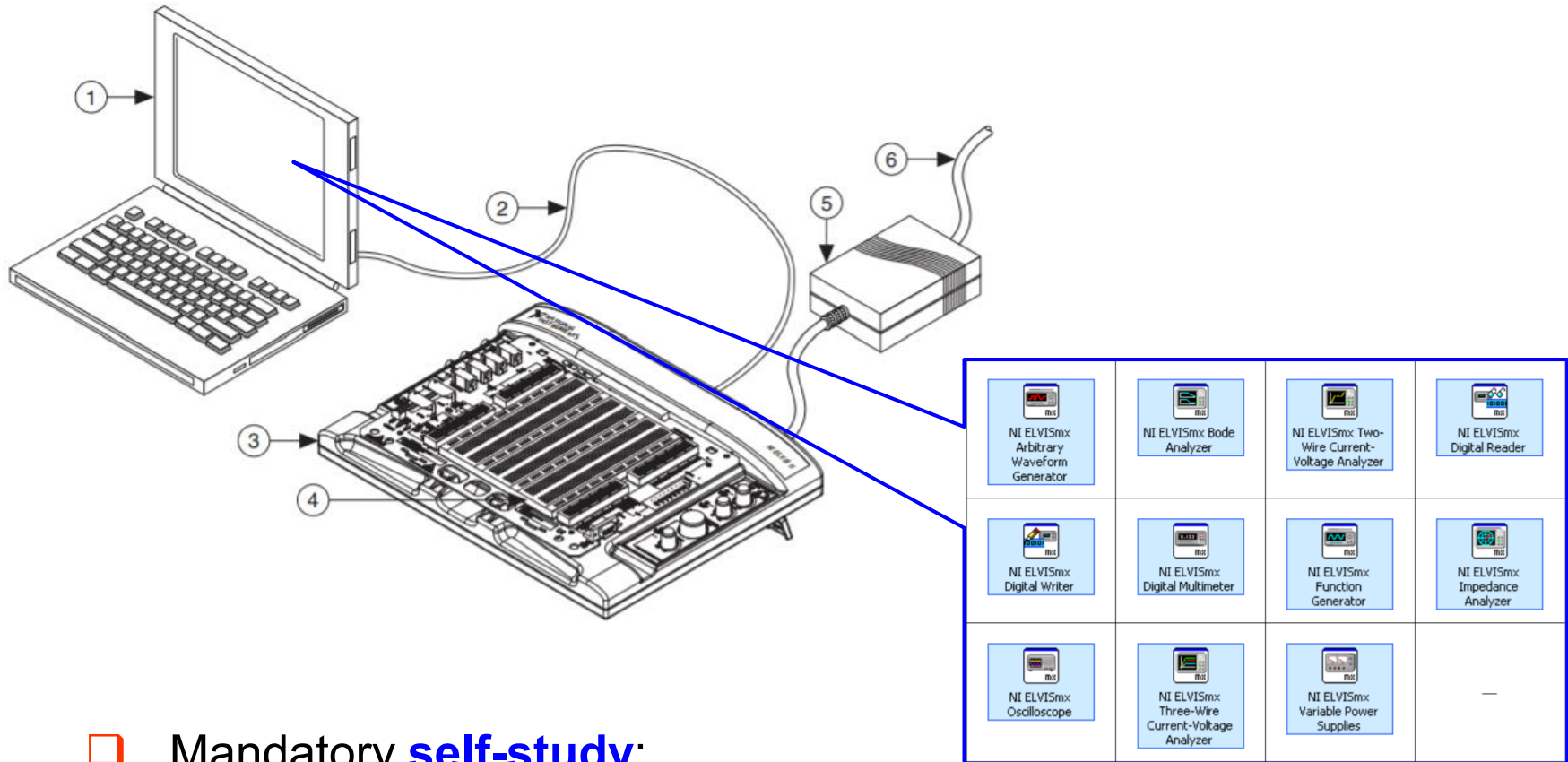
The NI ELVIS II+ DAQ system and LabView programming language



❑ Mandatory **self-study**:

- Uploaded materials on the course website
- <https://www.ni.com/getting-started/labview-basics/>


The NI ELVIS II+ DAQ system

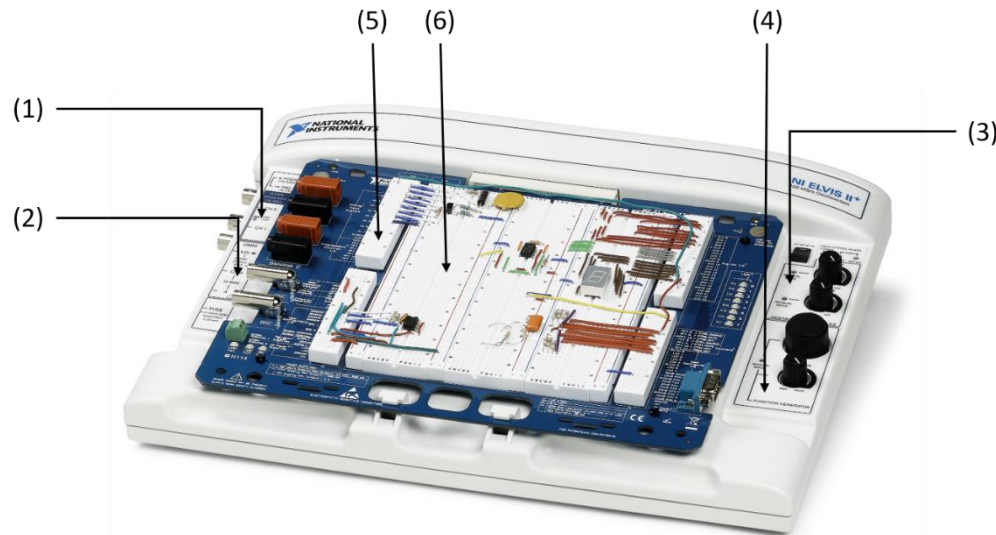

❑ Some specs/functionalities:




- 8 differential or 16 single ended analog input channels, 16-bit ADC
- 24 digital I/O channels
- 15 PFIs (programmable function interface)
- Waveform Generator/Analog Output, 16-bit DAC
- 2 General Purpose Counter/Timers
- PC interfacing via USB port

Software

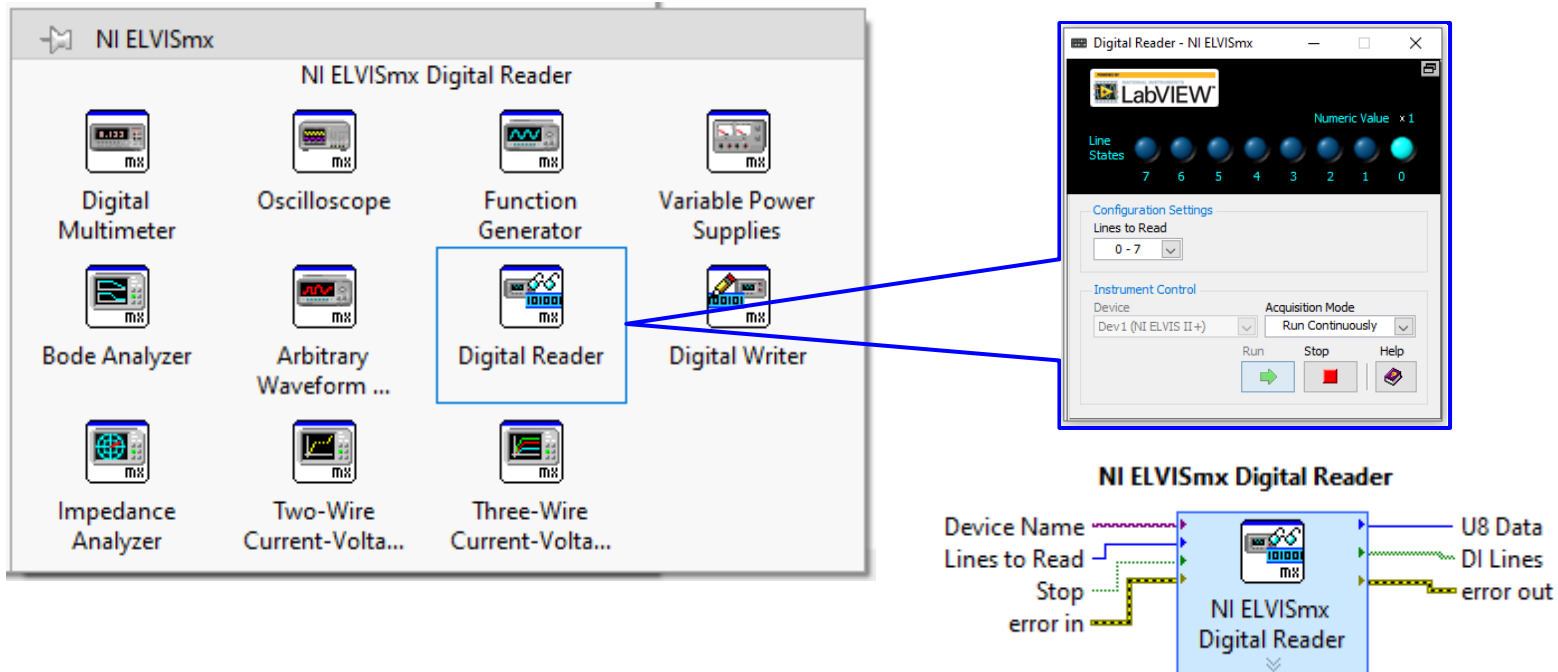

- ❑ DAQ functionalities can be programmed via LabVIEW
 - Running on Windows PC
 - The main control GUI is called NI ELVISmx, which provides many Soft Front Panels, e.g., Digital Multimeter (DMM), Bode Analyzer, Oscilloscope, Function Generator, Digital Reader/Writer, ...
 - LabView is a (relatively) simple graphical HLL

Examples

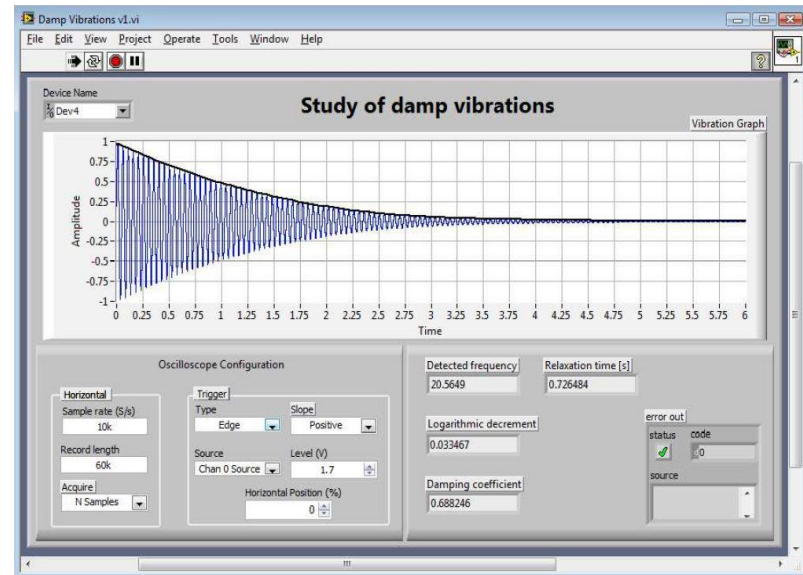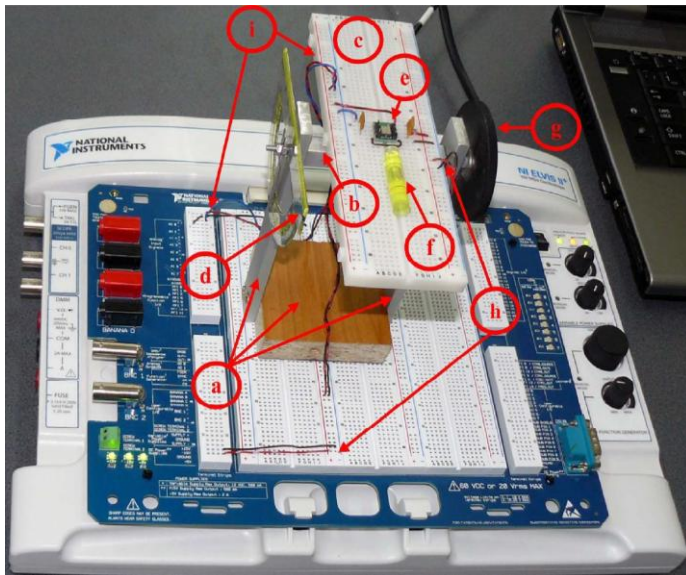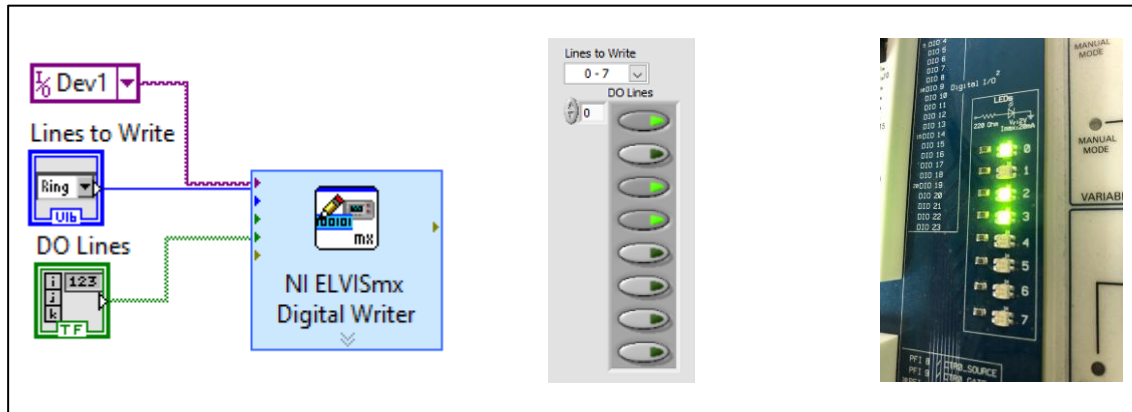

Summary

- ❑ Principles of a DAQ board
 - A/D process: sampling, quantization, encoding
 - Common A/DC converters
 - D/A process
 - R/2R ladder DAC
- ❑ Introduction to NI ELVISII+ DAQ board
- ❑ **Self-study:** NI ELVISII manual + Getting started with LabView
- ❑ **Next lecture:** I/O interfacing with computer